

Formulas:

$$A_v = \frac{g_{m1} g_{m6}}{g_{o1} g_{o6}} = 223,87$$

$$\times C_H = 1,25 \text{ pF}$$

$$\times \text{GBW}_g = \frac{g_{mPQ}}{2\pi C_H} = \frac{g_{m1}}{2\pi C_H} = 17000 \rightarrow \text{get } g_{m1}$$

$$\times P_Q = \frac{g_{m6}}{C_L} \approx 3 \text{ GBW} \rightarrow \text{get } g_{m6}$$

$$\times C_H = \frac{C_L}{4} = 1,25 \text{ pF}$$

$$g_{o4} \ll g_{o1} \text{ and } g_{o5} \ll g_{o6}$$

$$\mu_1 = \mu_2 \text{ and } \mu_3 = \mu_4$$

$$\times C_L = 5 \text{ pF}$$

$$\Rightarrow g_{m6} = 3 \cdot 17000 \cdot 2\pi \cdot 5 \cdot 10^{-12} \\ = 1,6022 \cdot 10^{-6}$$

$$\Rightarrow g_{m1} = 17000 \cdot 2\pi \cdot 1,25 \cdot 10^{-12} \\ = 1,3352 \cdot 10^{-7}$$

$$\Rightarrow g_{o1} \cdot g_{o6} = \frac{g_{m1} \cdot g_{m6}}{223,87} = \frac{1,6022 \cdot 10^{-6} \cdot 1,3352 \cdot 10^{-7}}{223,87} \\ = 9,5557 \cdot 10^{-16}$$

Voltage drops V_{DS} over transistors:

$$V_{M1} = -0,336V = V_{M2} \rightarrow p$$

$$V_{M3} = 0,336V = V_{M4} \rightarrow n$$

$$V_{M7} = -0,336V \rightarrow p$$

$$V_{M8} = -0,550V = V_{M5} \rightarrow p$$

$$V_{M6} = 0,550V \rightarrow n$$

Get g_{o1} and $g_{o6} \rightarrow$ want most gain first stage:

\rightarrow assume $V_{ov} = 0V$ for all

\rightarrow gain of 223,87

\Rightarrow first stage gain of 46,546 \rightarrow choose $L = 1000n$

$$\Rightarrow \frac{g_{m1}}{g_{o1}} = 46,546 \Rightarrow g_{o1} = \frac{g_{m1}}{46,546} = 2,8685 \cdot 10^{-9}$$

$$\Rightarrow \text{gain second stage} \approx \frac{223,87}{46,546} = 4,8097$$

$$\Rightarrow \frac{g_{m6}}{g_{o6}} = 4,8097 = 4,99426 \Rightarrow \text{lowest value pickable}$$

\rightarrow adds buffer \downarrow
 $L = 60n$

$$\Rightarrow g_{o6} = \frac{g_{m6}}{4,99426} = 2,0042 \cdot 10^{-7}$$

$$I_{D1} = \frac{g_{m1}}{22,2450} = 6,0021 \cdot 10^{-9}$$

$$I_{D6} = \frac{g_{m6}}{11,3299} = 1,4141 \cdot 10^{-7}$$

All current from $M1$ flows into $M4$ at DC

All current from $M2$ flows into $M3$

$$\text{current through } M7 = I_{D1} + I_{D2} = 2 \cdot I_{D1}$$

All current through $M6$ goes through $M5$ at DC

Current through M_7 comes from current mirror M_8

$$\Rightarrow \text{choose } I_{D8} = I_{D6} = 1,4141 \cdot 10^{-7}$$

$$\Rightarrow \text{then } I_{BIAS} = 1,4141 \cdot 10^{-7}$$

\Rightarrow good current sources are long transistors

$$\rightarrow \text{choose } L = 500 \text{ nm for } M_8 \text{ and } M_5$$

$$\Rightarrow \text{then is } L \text{ of } M_7 \text{ equal to } \frac{L_8}{\frac{I_{D7}}{I_{D8}}} = 5,8802 \cdot 10^{-6}$$

\Rightarrow NOTE Width of M_7 is equal to width of M_8 and is equal to $10 \cdot L_8$

Next: sizing M_3 and M_4

\Rightarrow again current mirror

$$\rightarrow L = 500 \text{ nm}$$

$$\Rightarrow \frac{g_{m4}}{I_{D4}} = 27,5157$$

$$\Rightarrow \frac{g_{m4}}{g_{o4}} = 27,6 \Rightarrow g_{o4} = \frac{g_{m4}}{27,6}$$

\Rightarrow After iteration \Rightarrow gain and bandwidth not big enough

\Rightarrow to do:

\rightarrow calculate V_{cm} , V_{out} and P_{diss} \rightarrow get from V_{in} and I_{in}

\rightarrow calculate g_{o4} of $M_{5,8}$ and M_7 (for g_{o4} plot)

\rightarrow calculate $V_{ds, sat}$

\rightarrow new iteration with higher gain and GBW

\rightarrow figure out how to use R_{in} in calculations