

Formulas:

$$A_v = \frac{g_{m1} g_{m6}}{g_{o1} g_{o6}} = 223,87$$

$$\times C_H = 1,25 \text{ pF}$$

$$\times \text{GBW}_g = \frac{g_{mPQ}}{2\pi C_H} = \frac{g_{m1}}{2\pi C_H} = 17000000 \rightarrow \text{get } g_{m1}$$

$$\times P_Q = \frac{g_{mb}}{C_A} \approx 3 \text{ GBW} \rightarrow \text{get } g_{mb}$$

$$\times C_H = \frac{C_L}{4} = 1,25 \text{ pF}$$

$$g_{o4} \ll g_{o1} \text{ and } g_{o5} \ll g_{o6}$$

$$\mu_1 = \mu_2 \text{ and } \mu_3 = \mu_4$$

$$\times C_L = 5 \text{ pF}$$

$$\Rightarrow g_{mb} = 3 \cdot 17000000 \cdot 2\pi \cdot 5 \cdot 10^{-12} \\ = 0,0016$$

$$\Rightarrow g_{m1} = 17000000 \cdot 2\pi \cdot 1,25 \cdot 10^{-12} \\ = 1,3352 \cdot 10^{-4}$$

$$\Rightarrow g_{o1} \cdot g_{o6} = \frac{g_{m1} \cdot g_{mb}}{223,87} \\ = 9,5425 \cdot 10^{-10}$$

Voltage drops V_{DS} over transistors:

$$V_{M1} = -0,336V = V_{M2} \rightarrow p$$

$$V_{M3} = 0,336V = V_{M4} \rightarrow n$$

$$V_{M7} = -0,336V \rightarrow p$$

$$V_{M8} = -0,550V = V_{M5} \rightarrow p$$

$$V_{M6} = 0,550V \rightarrow n$$

Get g_{o1} and $g_{o6} \rightarrow$ want most gain first stage:

\rightarrow assume $V_{ov} = 0V$ for all

\rightarrow gain of 223,87

\Rightarrow first stage gain of 46,546 \rightarrow choose $L = 1000n$

$$\Rightarrow \frac{g_{m1}}{g_{o1}} = 46,546 \Rightarrow g_{o1} = \frac{g_{m1}}{46,546} = 2,8685 \cdot 10^{-9}$$

$$\Rightarrow \text{gain second stage} \approx \frac{223,87}{46,546} = 4,8097$$

$$\Rightarrow \frac{g_{m6}}{g_{o6}} = 4,8097 = 4,88426 \Rightarrow \text{lowest value pickable}$$

\rightarrow adds buffer \downarrow
 $L = 60n$

$$\Rightarrow g_{o6} = \frac{g_{m6}}{4,88426} = 2,0042 \cdot 10^{-7}$$

$$I_{D1} = \frac{g_{m1}}{22,2450} = 6,0021 \cdot 10^{-9}$$

$$I_{D6} = \frac{g_{m6}}{11,3299} = 1,4141 \cdot 10^{-7}$$

All current from $M1$ flows into $M4$ at DC

All current from $M2$ flows into $M3$

$$\text{current through } M7 = I_{D1} + I_{D2} = 2 \cdot I_{D1}$$

All current through $M6$ goes through $M5$ at DC

Current through M_7 comes from current mirror M_8

\Rightarrow choose $I_{D8} = I_{D6} = 1,4141 \cdot 10^{-7}$

\Rightarrow then $I_{BIAS} = 1,4141 \cdot 10^{-7}$

\Rightarrow good current sources are long transistors

\rightarrow choose $L = 500 \text{ nm}$ for M_8 and M_5

\Rightarrow then is L of M_7 equal to $\frac{L_8}{\frac{I_{D7}}{I_{D8}}} = 5,8802 \cdot 10^{-6}$

\Rightarrow NOTE Width of M_7 is equal to width of M_8 and is equal to $10 \cdot L_8$

Next: sizing M_3 and M_4

\Rightarrow again current mirror ($g_{o4} < g_{o2}$) ∇

\Rightarrow rechoose M_2 to get $g_{o2} \gg g_{o4}$

$L_2 = 500 \text{ nm} \Rightarrow$ gain stage $1 = 27$

$\hookrightarrow V_{ov2} = -0,1 \text{ V} \Rightarrow g_{o2} \approx 0,5$

\Rightarrow rechoose $V_{ov6} = 0,1 \text{ V}$

\Rightarrow After iteration \Rightarrow gain and bandwidth not big enough

\Rightarrow to do:

\rightarrow calculate V_{cm} , V_{out} and P_{diss} \rightarrow get from V_{in} and I_{in}

\rightarrow calculate g_{o5} of $M_{5,8}$ and M_7 (V_{ov} , g_{o5} plot)

\rightarrow calculate $V_{ds, sat}$

\rightarrow new iteration with higher gain and GBW

\rightarrow figure out how to use R_{in} in calculations

\hookrightarrow use zero to compensate slowest pole?

\rightarrow validate that $g_{o5} < g_{o6}$ and $g_{o4} < g_{o1}$

$$\begin{aligned}
 V_{cm, in, max} &= V_{T2} + V_{T4} + V_{OV4} + V_{DD} \\
 &= (V_{OV2} - V_{GS2}) + (V_{OV4} - V_{GS4}) + V_{OV4} + V_{DD} \\
 &= -V_{GS2} - V_{GS4} + V_{DD} \\
 &= 1,0320 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{cm, in, min} &= V_{OV7} + V_{OV2} + V_{T2} \\
 &= V_{OV7} + V_{OV2} + V_{OV2} - V_{GS2} \\
 &= 0 + 0 + 0 - V_{GS2} \\
 &= 0,0220 \text{ V}
 \end{aligned}$$

V_{out} :

$$V_{DSAT6} \leq V_{out} \leq V_{DD} - V_{DSAT5}$$

$$\Rightarrow V_{GS4} - V_{T4} \leq V_{out} \leq V_{DD} - V_{GS5} - V_{T5}$$

$$\Rightarrow V_{GS4} - (V_{OV4} - V_{GS4}) \leq V_{out} \leq V_{DD} - V_{GS5} - (V_{OV5} - V_{GS5})$$

$$\Rightarrow 2V_{GS4} - V_{OV4} \leq V_{out} \leq V_{DD} - V_{OV5}$$

$$\Rightarrow \begin{cases} V_{out, max} = V_{DD} - V_{OV5} = 1,1 \text{ V} \\ V_{out, min} = 2 \cdot V_{GS4} - V_{OV4} = 0,18 \text{ V} \end{cases}$$

P_{diss} ?

\Rightarrow equal to $V_{in} \cdot I_{in}$?

$$\Rightarrow P_{diss} = 1,1 \text{ V} \cdot I_{BIAS} + 1,1 \text{ V} \cdot I_{DS7} + 1,1 \text{ V} \cdot I_{DS5}$$

$$S = \frac{g_m}{C_m} = \frac{1}{R_m C_m}$$

Next: ~~Do~~ recalculation with
 $\frac{g_{m1}}{g_{o1} + g_{o3}}$ and $\frac{g_{m6}}{g_{o6} + g_{o3}}$

~~→ cannot
small enough
assume $g_{o1} \approx g_{o3}$~~

get g_{o3} and g_{o5}

~~→ choose L_3, L_4 and L_5 based on their g_o~~

~~→ do new iteration~~

~~→ choose R_H small enough to shift pole far
enough from dominant pole~~

→ How to increase g_o → increase length
decrease g_o → decrease length
→ increase γ_{gs} → increase γ_{ov}

→ ERROR in GBW

New Iteration

$$\frac{g_{m1}}{g_{01} + g_{03}} \approx \frac{g_{m1}}{2 \cdot g_{01}} \rightarrow \text{choose double the wanted gain from plot}$$

$$\frac{g_{mb}}{2g_{06}} \rightarrow \text{Same}$$

$$\Rightarrow \frac{g_{m1}}{2g_{01}} \approx 60 \Rightarrow \text{choose } 48,5$$

$$\Rightarrow \text{for } M1: V_{ov} = 1 \text{ and } L = 1500 \text{ nm}$$

$$\Rightarrow 2g_{01} = \frac{g_{m1}}{48,5} =$$

$$\Rightarrow \text{choose } L_2 = 100 \text{ nm}$$

$$\text{and } V_{ov} = -0,36 \text{ V}$$

$$\Rightarrow \frac{g_{m3}}{g_{03}} = 14,23 \Rightarrow g_{m3} = 14,33 \cdot g_{03}$$

$$\frac{g_{mb}}{2g_{06}} \approx 20$$

$$\Rightarrow \text{for } M6: V_{ov} = 0 \quad \text{gain of } 22,28 \text{ for } L = 200 \text{ nm}$$

$$\Rightarrow g_{06} = \frac{g_{mb}}{20} \cdot \frac{1}{2} = g_{05}$$

$$\Rightarrow V_{ov5} =$$

New Attempt

M1 and M2 \rightarrow increase q_{o1} and q_{o2}

choose $V_{ov} = -0,2V$ and $L = 1000 \text{ nm}$

$$\Rightarrow \frac{g_{m1}}{q_{o1}} = \frac{24,75}{18,2}, \quad \frac{g_{m1}}{I_{D51}} = \frac{13,75}{8,45}, \quad V_{GS} = -0,42$$

$$\Rightarrow \text{gain for stage 2: } \frac{6,423}{11,6589}$$

M6

choose $V_{ov} = 0,2V$ and $L = 60 \text{ nm}$

$$\Rightarrow \frac{g_{m6}}{q_{o6}} = \frac{7}{13,6}, \quad \frac{g_{m6}}{I_{D56}} = \frac{5,3}{6,95}, \quad V_{GS} = 0,56$$

$$\Rightarrow \text{total gain} = 243,2500$$

M3 and M4

$\Rightarrow V_{ov} = -0,1V$ \rightarrow to decrease q_{o3} and q_{o4}

\Rightarrow take $L = 60 \text{ nm}$ to decrease q_{o3} and q_{o4}

$$\Rightarrow \frac{g_{m3}}{I_{D53}} = \frac{18}{23,1} \Rightarrow g_{m3} = I_{D53} \cdot \frac{18}{23,1}$$

$$\frac{g_{m3}}{q_{o3}} = \frac{7,3}{7,6} \quad V_{GS} = 0,21$$

M5

$\Rightarrow V_{ov} = 0,2V$ and $L = 60 \text{ nm}$

\rightarrow decrease q_{o5}

$$\frac{g_{m5}}{q_{o5}} = 10,25$$

$$V_{GS} = -0,17$$

\Rightarrow change all V_{ov} to $\pm 0,2V$

→ fix stage 2. ⇒ get right gain from Matlab ⇒ figure out mistake

Aim for gain of 10 for second stage and reduce g_{05}

⇒ $\frac{g_{m6}}{g_{06}} \approx 10 \Rightarrow$ from plot $V_{ov} = 0,4$ $L = 100 \text{ nm}$

$$g_{06} = \frac{g_{m6}}{10} = 1,6 \cdot 10^{-4}$$

$$g_{m6} = 0,0016$$

$$\frac{g_{m6}}{I_{D6}} = 3,55 \Rightarrow I_{D6} = \frac{g_{m6}}{3,55} = 4,507 \cdot 10^{-4}$$

$$V_{DS6} = 0,71$$

$$\frac{W}{L} = 10 \quad n = 10 \cdot L$$

g_{05}

⇒ $I_{D5} = I_{D6} = 4,507 \cdot 10^{-4}$ for DC

⇒ choose $V_{ov} = 0,2 \text{ V}$ and $L = 100 \text{ nm}$ to reduce g_{05}

⇒ $\frac{g_{m5}}{g_{05}} = 23,5$ and $\frac{g_{m5}}{I_{D5}} = 26,5$

⇒ $V_{GS5} = -0,14$

Aim for second stage: gain of 10

assume $v_{inter} \approx 0,336 \text{ V}$

⇒ and $v_{out} \approx 0,550 \text{ V}$

⇒ $V_{DS6} = 0,550 \text{ V}$

$$V_{GS6} = V_{DS6} - V_{ov} = 0,550 \text{ V} - 0,336 \text{ V} = 0,214 \text{ V}$$

⇒ $\frac{g_{m6}}{g_{06}} = 16,9$ and $\frac{g_{m6}}{I_{D6}} = 25,4$ $L = 80 \text{ nm}$

⇒ for g_{15} : $V_{GS5} = -0,550 \text{ V} = V_{DS5}$ $I_{D5} = I_{D6} = 6,300 \cdot 10^{-5}$

what we know: $g_{m6} = 0,0016 = 1,6 \cdot 10^{-3}$
 $g_{m1} = 13352 \cdot 10^{-4}$

Stage 2

assume $V_{ov7} = V_{ov5} = V_{ov8} = -0,2V$

$V_{DS6} = 0,550V \Rightarrow$ voltage divided over r_{15} and r_{16}

gain of 20 in second stage

make $g_{o5} \ll g_{o6}$ by making $V_{ov5} = 0,2$ and $V_{ov6} = 0,48$

\Rightarrow if $g_{m6} = 1,6 \cdot 10^{-3} \Rightarrow$ choose $V_{ov6} = 0,48$
 and $L_6 = 1000 \text{ nm}$

$$\Rightarrow \frac{g_{m6}}{g_{o6}} = 16,7 \Rightarrow g_{o6} = 9,5808 \cdot 10^{-5}$$

$$\Rightarrow \frac{g_{m6}}{I_{DS6}} = 4,55 \Rightarrow I_{DS6} = \frac{g_{m6}}{4,55} = 3,5165 \cdot 10^{-4}$$

$$\Rightarrow I_{DSS} = I_{DS6}$$

\Rightarrow in order to get $g_{o5} \ll g_{o6} \Rightarrow$ choose $V_{ov5} = 0,2V$
 choose $L_5 = 1000 \text{ nm} \Rightarrow$ current source

is not possible due to high I_{DS6}

$$\Rightarrow \text{gain second stage} = \frac{g_{m6}}{g_{o5} + g_{o6}}$$

\Rightarrow try to get $g_{o5} \approx g_{o6}$ by making them almost identical

$$\Rightarrow V_{ov5} = -0,48V$$

$$\Rightarrow \text{gain second stage} = 8,0678$$

First Stage

$$g_{m1} = 1,3352 \cdot 10^{-4}$$

$$\text{gain first stage: } \frac{g_{m1}}{g_{o1} + g_{o2}}$$

$$\Rightarrow \text{wanted gain} = \frac{223,87}{8,0678} = 27,7486$$

$$\Rightarrow \text{choose } L_1 = 1000 \text{ nm} \Rightarrow V_{ov1} = -0,1 \text{ V}$$

$$\frac{g_{m1}}{g_{o1}} = 34,5 \Rightarrow g_{o1} = 3,8701 \cdot 10^{-6}$$

$$\frac{g_{m1}}{I_{DS1}} = 13,7 \Rightarrow I_{DS1} = 9,7460 \cdot 10^{-6}$$

$$I_{DS3} = I_{DS1}$$

$$\text{for } \frac{g_{m1}}{g_{o1} + g_{o3}} \approx 27,74 \Rightarrow g_{o3} = \frac{g_{m1}}{27,74} - g_{o1} \\ = 8,4317 \cdot 10^{-7}$$

$$\Rightarrow \text{For } M_3: \text{choose } L_3 = 1000 \text{ nm and } V_{ov} = -0,1 \text{ V}$$

$$\hookrightarrow \text{identical to } M_1 \Rightarrow A_{V1} \approx \frac{g_{m1}}{2g_{o1}}$$

\Rightarrow Next iteration \Rightarrow choose g_{m6} and then choose C_M

$$\hookrightarrow \text{why } \frac{g_{m1}}{3 \cdot g_{o1}}$$

How to get $g_{o4} \leftarrow g_{o2}$

\Rightarrow make v_{ds2} small and v_{gs4} bigg

\Rightarrow choose $v_{ds4} = 0,55V$ and $v_{ds2} = -0,2V$

and $v_{ds4} = -0,45V$

π_1 and π_2

$$g_{m1} = 1,3352 \cdot 10^{-4} \Rightarrow \gamma_{o1} = -0,114V$$

$$\Rightarrow \text{gain}_1 = \frac{g_{m1}}{g_{o1}} = 17,5 \quad L_1 = 1000n$$

$$\Rightarrow g_{o1} = 1,0682 \cdot 10^{-5}$$

$$\text{gain-eff} = \frac{g_{m1}}{I_{DS1}} = 12,65$$

$$\Rightarrow I_{DS1} = 1,0555 \cdot 10^{-5}$$

π_3 and π_4

$$I_{DS4} = I_{DS3} = I_{DS2} = I_{DS1}$$

choose $L = 1000nm$

$$V_{DS} = V_{GS} = 0,55V$$

\Rightarrow

New Iteration

→ second stage

$$\Rightarrow g_{m6} = 0,0016$$

we know: $V_{GS5} = -0,550V = V_{DS5} = V_{DS8}$

$$\text{if } v_{out} = 0,550V$$

$$\Rightarrow V_{DS6} = 0,550V$$

choose $L_6 = 1000 \text{ nm}$

$$\text{if } g_{m6} = 0,0016 \Rightarrow \text{then } V_{ov} = 0,48V$$

$$\Rightarrow \frac{g_{m6}}{g_{o6}} = 16,7 \Rightarrow g_{o6} = 9,5808 \cdot 10^{-5}$$

$$\Rightarrow \frac{g_{m6}}{I_{DS6}} = 4,54 \Rightarrow I_{DS6} = 3,5242 \cdot 10^{-4}$$

$$\text{For } M_5: I_{DS6} = I_{DS5}$$

* choose $L = 1000 \text{ nm}$ to reduce g_{os} as much as possible

⇒ from multCalc calculate width M_5 so correct g_{os} is obtained

$$\Rightarrow \text{gain stage 2: } \frac{g_{m6}}{g_{os} + g_{o6}} = 9,0856$$

$$\Rightarrow \text{gain needed for stage 1: } \frac{g_{\text{gain}}}{g_{m52}} = 24,6402$$

First stage

- gain of 24,64 is needed
- take $V_{gs7} = V_{gs8} = -0,550V$
 $V_{ds7} = -0,450$

→ reduce g_{o4}

- $L_4 = 1000 \text{ nm}$
 $V_{ds4} = 0,550V = V_{gs4}$

→ for M_1 & M_2

$$V_{ds1} = -0,2V$$

→ To include gain lowering effects of M_4 choose gain of 30

$$\Rightarrow \frac{g_{m1}}{g_{o1}} = 30 \quad \text{for } V_{ov1} = 0,05V \quad L_1 = 1000 \text{ nm}$$

$$\Rightarrow g_{m1} = 1,2 \cdot 10^{-5} \Rightarrow g_{o1} = 4 \cdot 10^{-7}$$

$$\Rightarrow \frac{g_{m1}}{I_{DS1}} = 26,4 \Rightarrow I_{DS1} = 4,5455 \cdot 10^{-7}$$

for M_3 & M_4

$$I_{DS3} = I_{DS4} = I_{DS1}$$

→ to accommodate $I_{DS1} \Rightarrow \text{Matlab has to be used to get } g_{o4} \text{ and } g_{m4}$

→ choose $L = 1000 \text{ nm}$ to minimize g_{o4}

→ total gain too low → increase gain stage 1

$$\Rightarrow V_{ov4} = 0,2 \text{ and } L = 1000 \text{ nm}$$

$$\Rightarrow \text{gain} = 36,4 \Rightarrow g_{m1} = 1,6 \cdot 10^{-5}$$

$$\Rightarrow g_{o1} = 4,3856 \cdot 10^{-7}$$

$$\Rightarrow \frac{g_{m1}}{I_{DS1}} = 33,26 \Rightarrow I_{DS1} = 4,8120 \cdot 10^{-7}$$

↳ lowers gain stage 1

$$\Rightarrow V_{gs6} = 0,650V$$

⇒ Gain stage 1 is OK according to LT spice ⇒ 24 dB

⇒ Gain stage 2: not OK

⇒ $v_{gs} = 0,650 \text{ V}$ ⇒ from stage 1

⇒ $L_6 = 1000 \text{ nH} \Rightarrow \text{gain} = 12,72$

⇒ $g_{mb} = 17,8 \cdot 10^{-3}$

⇒ $\frac{g_{mb}}{I_{DSS}} = 3,6 \Rightarrow I_{DSS} = 0,0049 \text{ A}$

⇒ If we want more gain from second stage

⇒ lower $v_{gs2} \Rightarrow$ lower v_{ds2}

$$350 + 0,2 + 0,650$$

~~$= 1,2$~~

